

Figure 30.1 The 4011-Type Quad 2-Input NAND Package

 


Figure 30.2 The Basic CMOS NAND Circuit

E1.1 The NAND Logic Function


- With 5 V supplied to IC pin 14, and pin 7 grounded, and with a DVM connected to node C (pin 3), apply all possible combinations of ground and +5V connections (4 of them) to inputs A, B (pins 1, 2). Prepare a truth table with columns A, B, C and entries of 0 and 5 (volts).
- ** • Join corresponding inputs of all four gates (all nodes A (pins 1, 6, 8, 13), and all nodes B (pins 2, 5, 9, 12)). Now run through all four input combinations, noting the corresponding output voltages at all four outputs (nodes C (nodes 3, 4, 10, 11)).

E1.2 Measurement of Propagation Delay



- Connect three of the NAND gates, with inputs joined, in a ring of 3, with the 4th NAND disabled with 1 input grounded. Using $\times 10$ probes, connect one channel of your oscilloscope to 1 of the gate outputs and the other to the next output along the ring.
- * • Please sketch the waveform and observe the phase relation to find possible delays

E2.0 Graphical Characterization

 

E2.1 Input, Transfer and Supply-Current Characterization

- With a 5 V supply voltage and 12 Vpp triangle-wave input at 1 kHz, connect inputs A and B together (pins 1, 2) to node I, and display voltages at nodes A and C in turn. Sketch and label the displays. Please find V_{th} .

E3.1 電路設計

- use chip of 4011 to implement NOT, AND, OR gate.