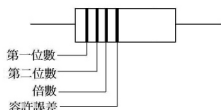


認識電阻



黑	棕	紅	橙	黃	綠	藍	紫	灰	白	金	銀
0	1	2	3	4	5	6	7	8	9	± 5%	± 10%

範例：

棕黑紅⇒ $10 \times 10^2 = 1000 \text{ ohm}$

紅紅棕⇒ $22 \times 10 = 220 \text{ ohm}$

認識電容



陶瓷電容(無極性)

101 : $10 \times 10^1 \text{ pF}$

102 : $10 \times 10^2 \text{ pF}$


103 : $10 \times 10^3 \text{ pF}$



電解電容(有極性)

長腳正極、短腳負極

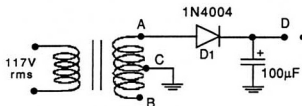E1.2 Half-Wave Rectifier with Capacitive Filter



- (a) Connect the circuit as shown in Fig. 5.3, and measure the voltages at A and D using your DVM on both its ac and dc ranges.
Now, with your oscilloscope whose channel gains and zero levels are equalized, measure nodes A and D.

- (b) Connect a 1 kΩ load from node D to ground and observe the voltages on nodes A and D with your "normalized" scope. Examine the ripple in some detail, with particular attention to the interval of diode conduction.

- While carefully examining the conduction interval, shunt the load by another 1 kΩ resistor intermittently. With a DVM connected to node D, note the small change in dc voltage which results.

- * • Now, with the original 1 kΩ still connected, shunt the output by a 1000 μF capacitor. Note: depending on its brand, type, age, and frequency of use, this large capacitor might exhibit considerable leakage (which may reduce if it is left connected for some time). Observe nodes A and D with your oscilloscope, and node D with your DVM set for dc measurement, while intermittently connecting an additional 1 kΩ load.

Consider the benefit of a large filter capacitor in reducing ripple amplitude and rising the output voltage. Compare your results with those implied by Eq. 3.36 in the Text.

E2.1 Full-Wave Operation Using a Center-Tapped Transformer

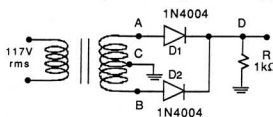


Figure 5.6 A Full-Wave Rectifier with Center-Tapped Transformer

- Assemble the circuit shown in Fig. 5.6, measuring nodes A and B, then nodes A and D, with the oscilloscope line-triggered and "normalized". Measure also the ac and dc voltages at node D using your DVM.
- While examining the waveform at A and D in some detail, connect a 100 Ω resistor intermittently from A to D. Note: be careful, it will get quite hot!

Consider the fact that both half cycles of the input sine wave are now employed. Verify the peak, average and RMS values of the voltage at D in comparison with that at A and/or B.

E3.1 A Full-Wave Bridge Without Filter

For purposes of comparison with previous experiments, we shall continue to use half the total available winding, as shown in Fig. 5.7.

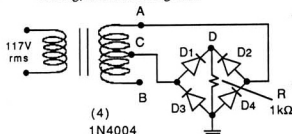


Figure 5.7 A Full-Wave Bridge with Resistor Load

- Connect the circuit as shown in Fig. 5.7, using your DVM to measure the ac and dc voltages between A and C, and between D and ground. Display the waveform at D on your oscilloscope.
- * • Repeat the measurements above with a 100 Ω resistor. Shunting R intermittently. Be aware that the power dissipation in the 100 Ω resistor in this situation is quite high. Do not hold its body in your fingers.

Consider these measurements in comparison to those for the centre-tapped full-wave scheme in exploration 2.1 above, noting the effect of extra diode drops. Use your DVM data to deduce the average diode drop that applies.

- ** • Repeat the previous explorations with the circuit of Fig. 5.7, but using transformer connections A and B. Be very careful with load heating.

Consider the relative reduction in importance of diode drops in your results.

