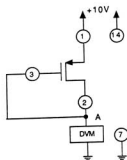


Figure 8.1 The CD4007 MOS Array

### E1.1 Measuring Device Thresholds



- connecting pins 2 and 14 momentarily.
- Measure the voltage from node A to ground (that is, read the DVM!). Estimate  $V_{tp}$ .

Figure 8.2 Measurement of  $V_t$  for a p-Channel Device

- \* Repeat the first of these measurements with drain and source interchanged (ie pin 2 as source and pin 1 as drain).
- Now, shunt the DVM with resistors of  $10k\Omega$  or less until the DVM reading lowers by a reasonable amount, say 1 V. Note that a convenient way to do this is to use a ( $10k\Omega$ ) potentiometer, whose setting is measured subsequently with an ohmmeter. Alternatively, a decade resistor box provides a self-calibrated alternative. Use Eq. 5.13 of the Text to find  $K_n$ .

### \*\* E1.4 N-Channel Device Parameters

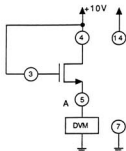


Figure 8.4 Measuring  $V_{tn}$  with a Non-Zero Source-to-Substrate Voltage

- First, measure  $V_{tn0}$  (almost) directly.
- Then, shunting the DVM by some appropriate resistor, say  $1k\Omega$ , find the device voltages, current, and then  $K$ .
- First, from DVM measurements made with pins 4 and 5 first shorted, then open, find  $V_{tn}$ .
- \* Then, shunt the DVM with a suitable resistor (perhaps  $1k\Omega$ ) and use the DVM reading to find device voltages, current and equivalent  $K_n$ .